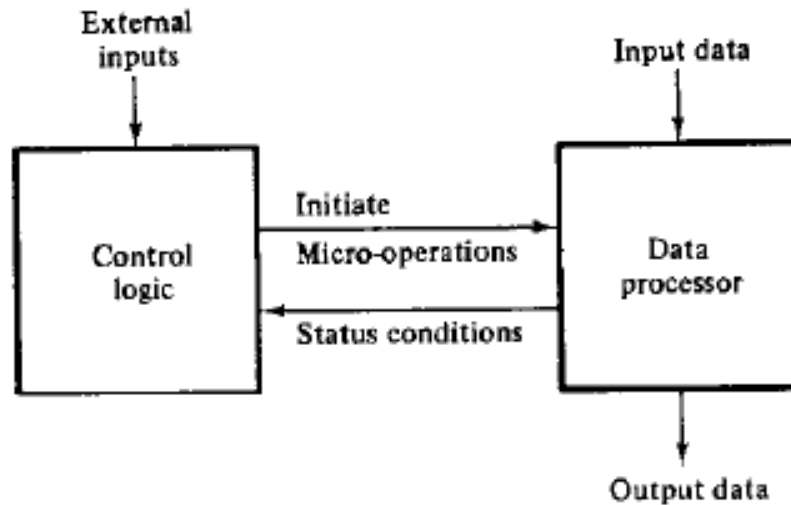


Control logic design

Module 6



- The control logic initiates all microoperations in data processor
- To execute instructions, the processor must have some means of generating the control signals needed in the proper sequence
- Done using sequential circuit whose internal states dictate the control functions of the system
- I.e., at any time, state of sequential control initiates a set of microoperations


Control organization

1. Hardwired control
 1. One flipflop per stage method
 2. Sequence register and decoder method
2. PLA control
3. Microprogrammed control

HARD WIRED CONTROL

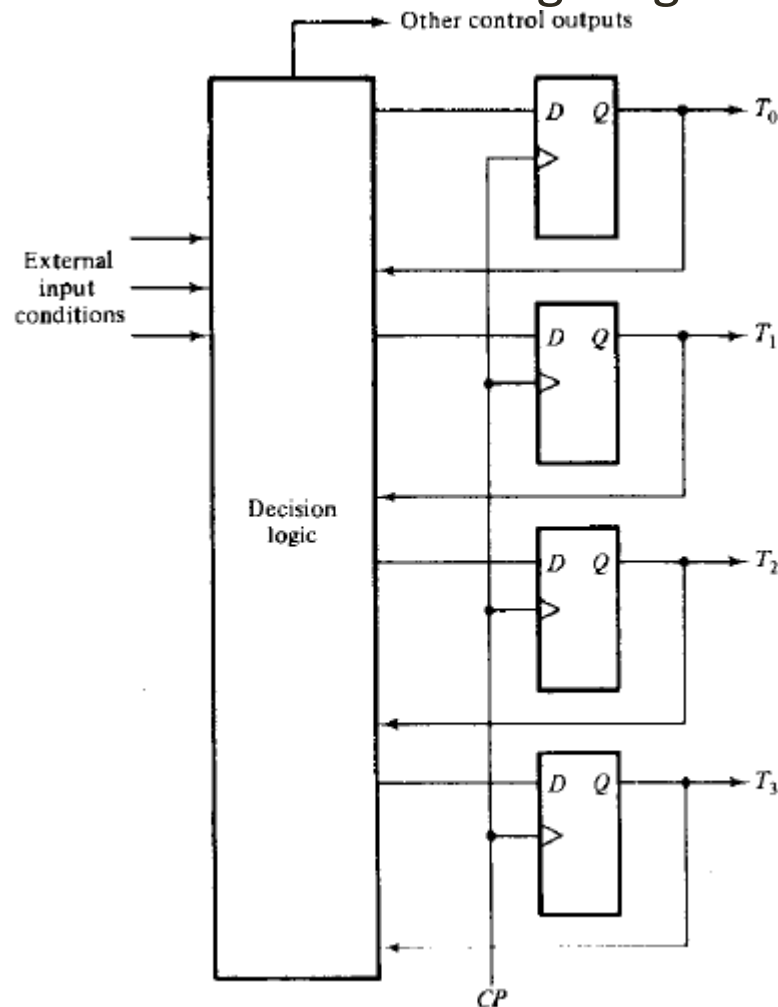1. One flip flop per stage


- One flip flop set at a time
- Single bit propagates under the control of design logic
- Each represents a state
- Transition: function of input and present T_i .



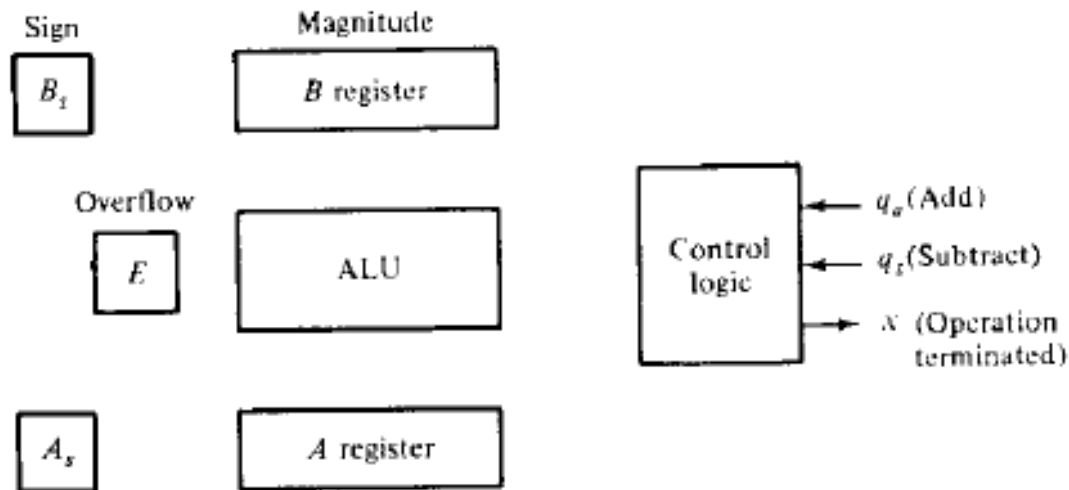
Example[Hardwired control-example1]

- Design carried out with 5 steps:
 1. Problem statement
 2. Initial equipment configuration
 3. Algorithm formulation
 4. Data processor part specification
 5. Design of control logic
- Problem statement: Addition and subtraction of binary fixed point numbers, negative numbers in sign's 2 complement form


- Equipment configuration:
 - Registers
 - A,B: numbers to be added/ subtracted stored in these reg
 - A_s, B_s : sign bits
 - E: 1 bit register storing overflow info
 - Input signals to control logic
 - q_a and q_b : add/subtract operation to be performed
 - Output signal
 - x : indicates end of operation



- Data processor part specification

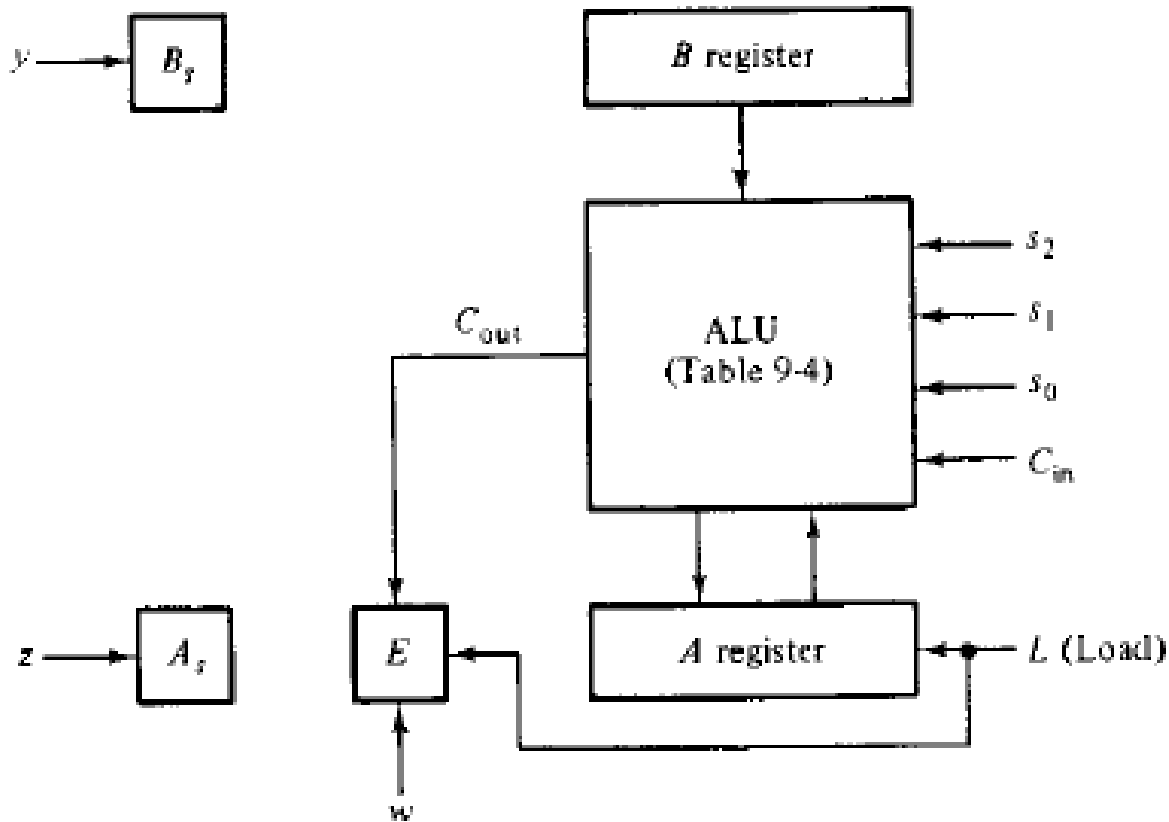


(a) Data processor registers and ALU

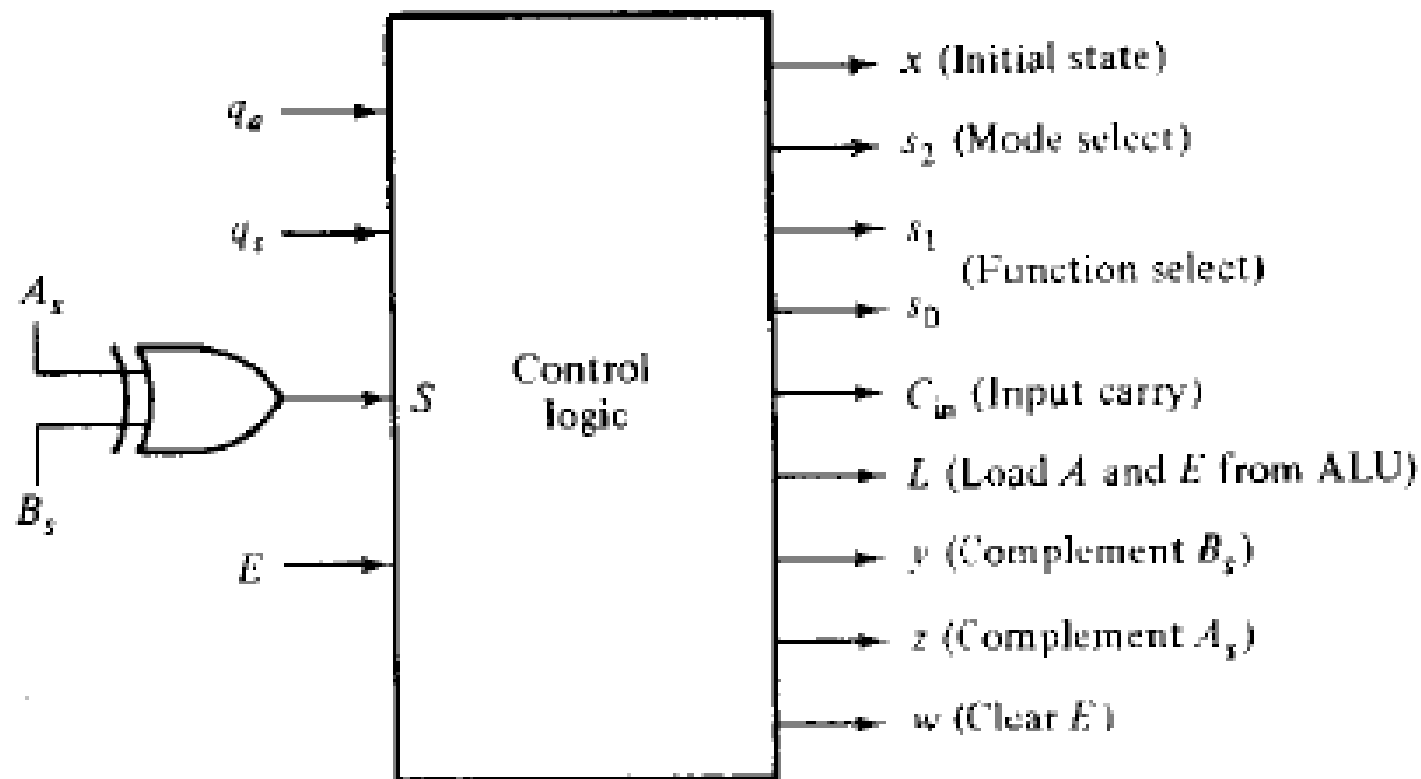


(b) Control block diagram

- Algorithm:

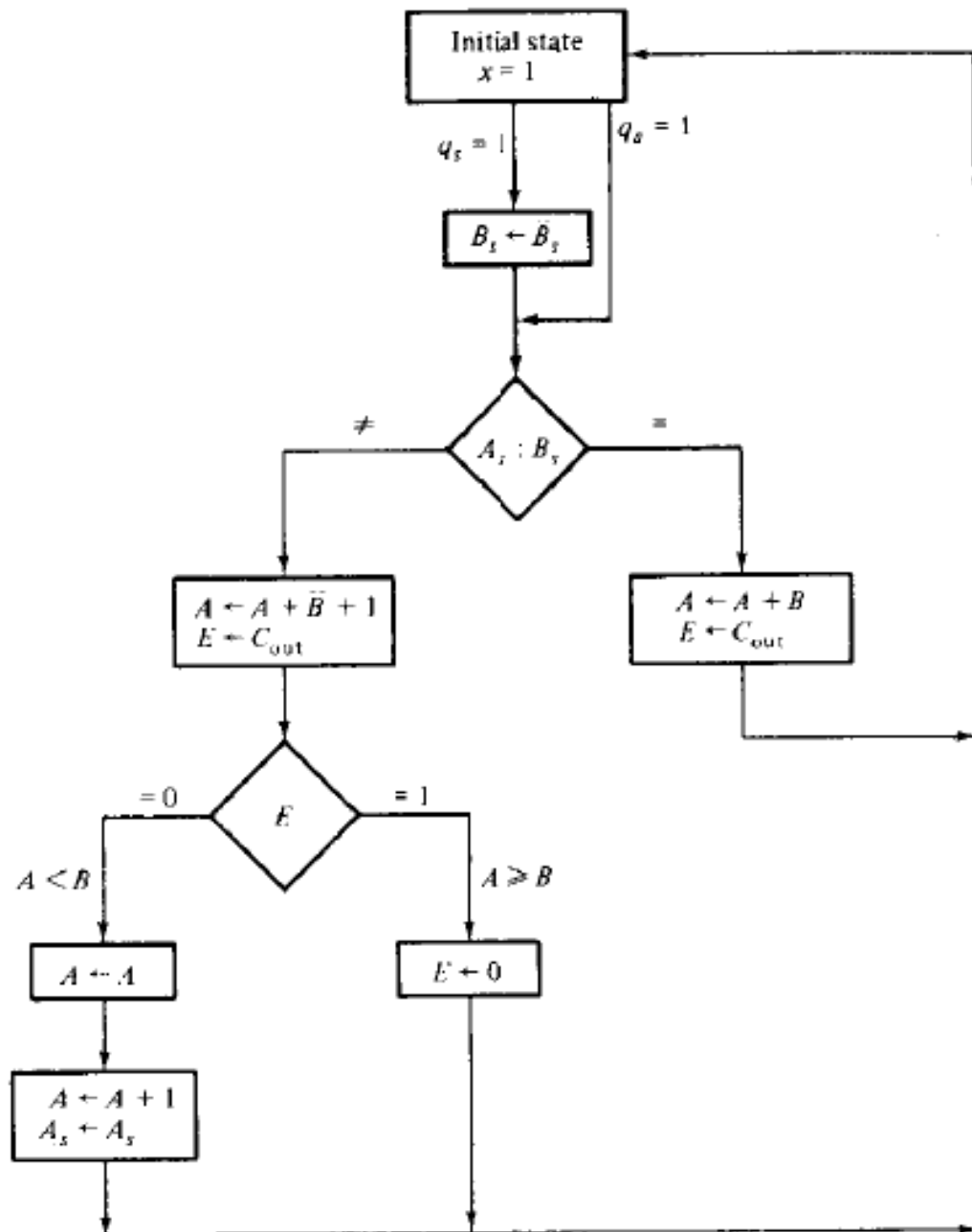

- Control state diagram

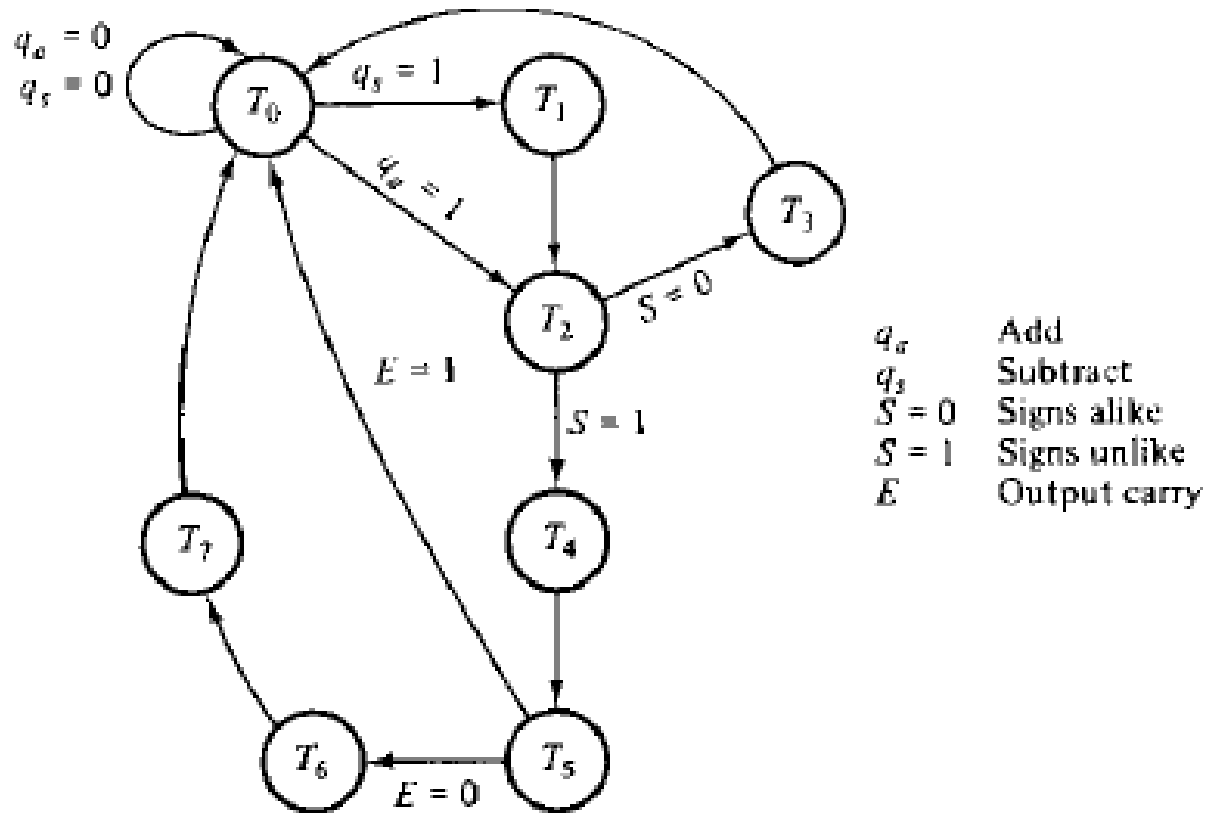

(a) State diagram

	Control outputs								
	x	s_2	s_1	s_0	C_{in}	L	y	z	w
T_0 : Initial state $x = 1$	1	0	0	0	0	0	0	0	0
T_1 : $B_s \leftarrow \bar{B}_s$	0	0	0	0	0	0	1	0	0
T_2 : nothing	0	0	0	0	0	0	0	0	0
T_3 : $A \leftarrow A + B$, $E \leftarrow C_{out}$	0	0	0	1	0	1	0	0	0
T_4 : $A \leftarrow A + \bar{B} + 1$, $E \leftarrow C_{out}$	0	0	1	0	1	1	0	0	0
T_5 : $E \leftarrow 0$	0	0	0	0	0	0	0	0	1
T_6 : $A \leftarrow \bar{A}$	0	1	1	1	0	1	0	0	0
T_7 : $A \leftarrow A + 1$, $A_s \leftarrow \bar{A}_s$	0	0	0	0	1	1	0	1	0


(b) Sequence of register transfers

- Design of hard wired control
 - 8 states are required as we have seen.
 - So 8 D flipflops used with the following input functions(implemented in decision logic)
 - At a time, any of the state will be active and corresponding D flipflop will be activated
 - The output signals are generated according to the boolean function(in table) using OR gate.

Flip-flop input functions	Boolean functions for output control
$DT_0 = q'_2 q'_3 T_0 + T_3 + ET_5 + T_7$	$x = T_0$
$DT_1 = q_3 T_0$	$s_2 = T_6$
$DT_2 = q_2 T_0 + T_1$	$s_1 = T_4 + T_6$
$DT_3 = S' T_2$	$s_0 = T_3 + T_6$
$DT_4 = ST_2$	$C_{in} = T_4 + T_7$
$DT_5 = T_4$	$L = T_3 + T_4 + T_6 + T_7$
$DT_6 = E' T_5$	$y = T_1$
$DT_7 = T_6$	$z = T_7$
	$w = T_5$

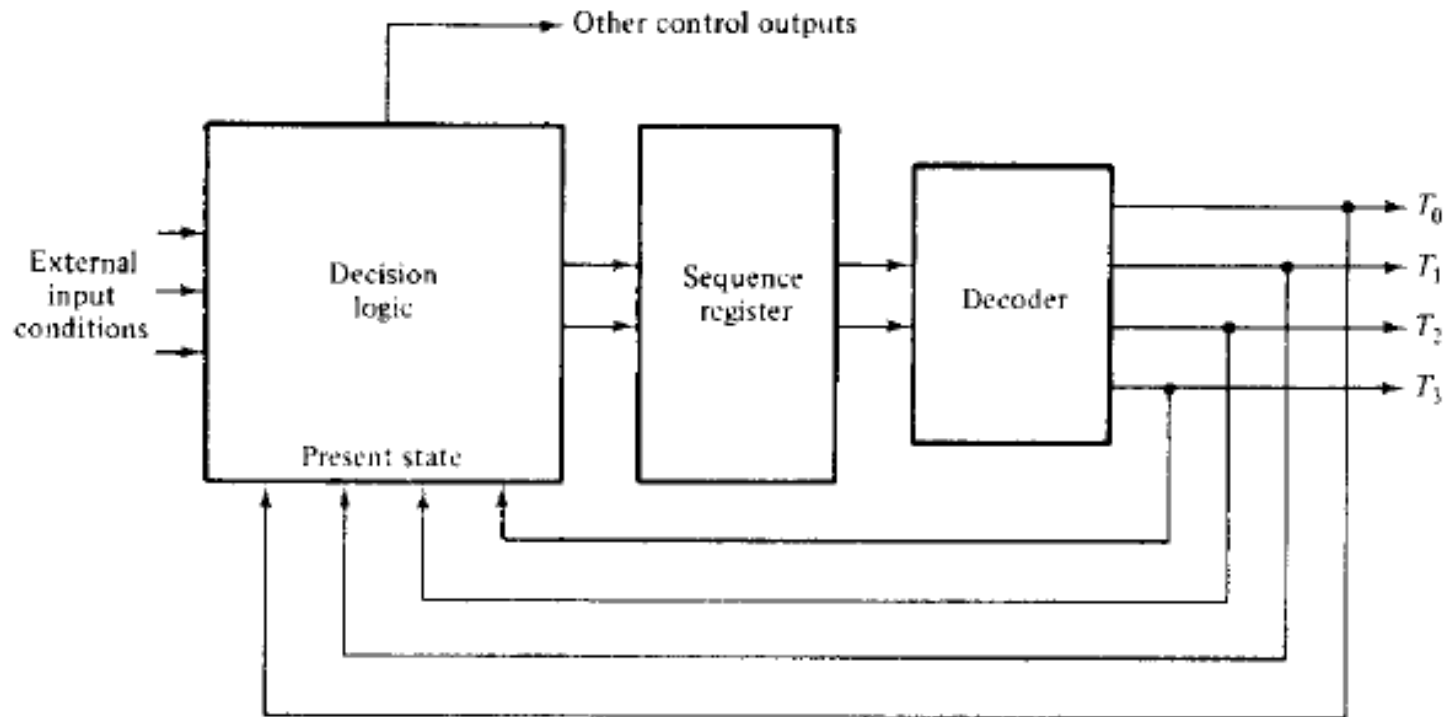2. Sequence register and decoder method

- Register: to sequence control states
- Register decoded to provide one output for each state



Example[Hardwired control-example2]

- Problem statement: To design an arithmetic circuit that multiplies two fixed point binary numbers in sign magnitude representation
- Equipment configuration:
 - Registers
 - B: to store multiplicand, Q-multiplier, A-partial product
 - A_s, B_s, Q_s : sign bits
 - P: counter(no of bits in the multiplier, decremented after formation of each partial product)
 - Input signals to control logic
 - q_m : operation to be performed
 - Output signal
 - Q_1 : rightmost bit in register Q



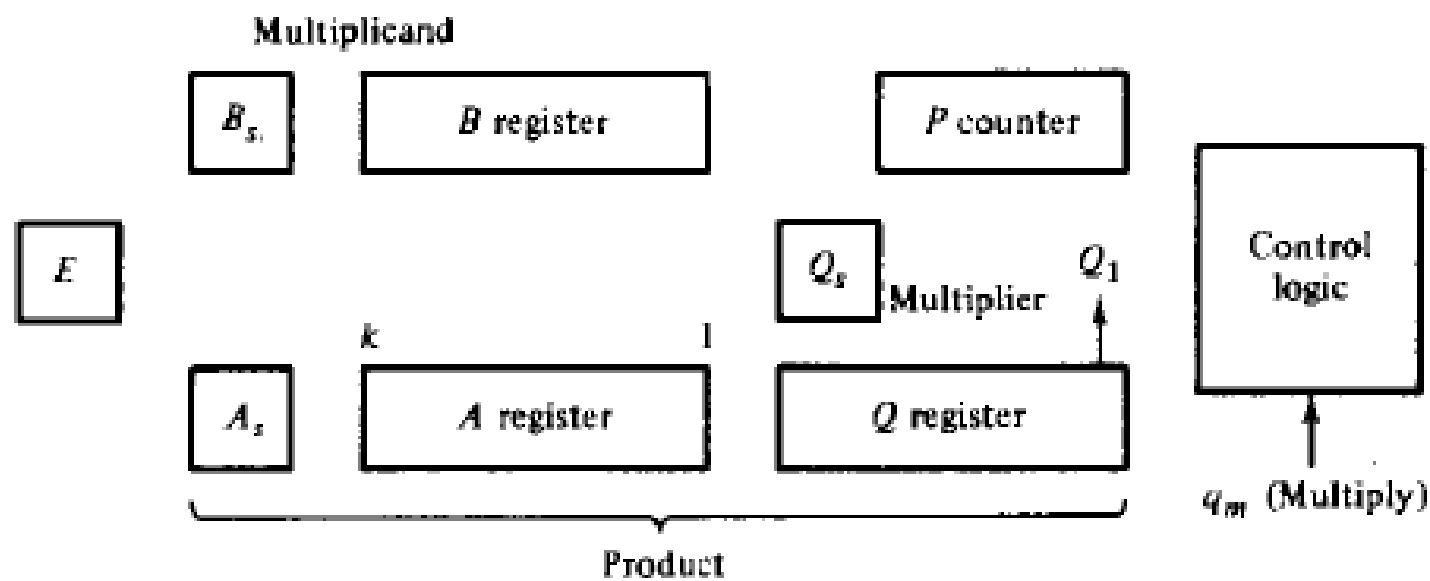



Figure 10-13 Registers for binary multiplier

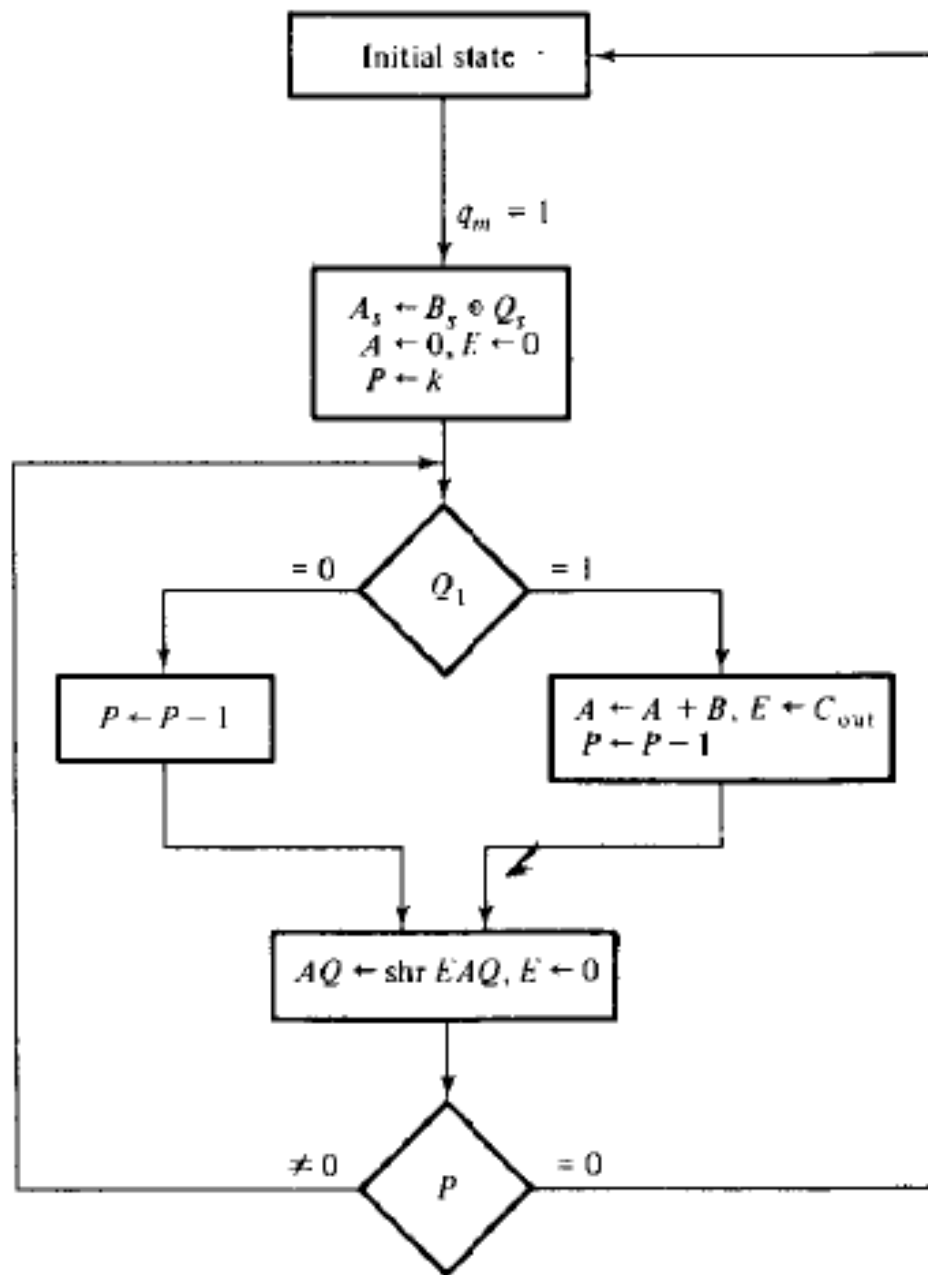

 

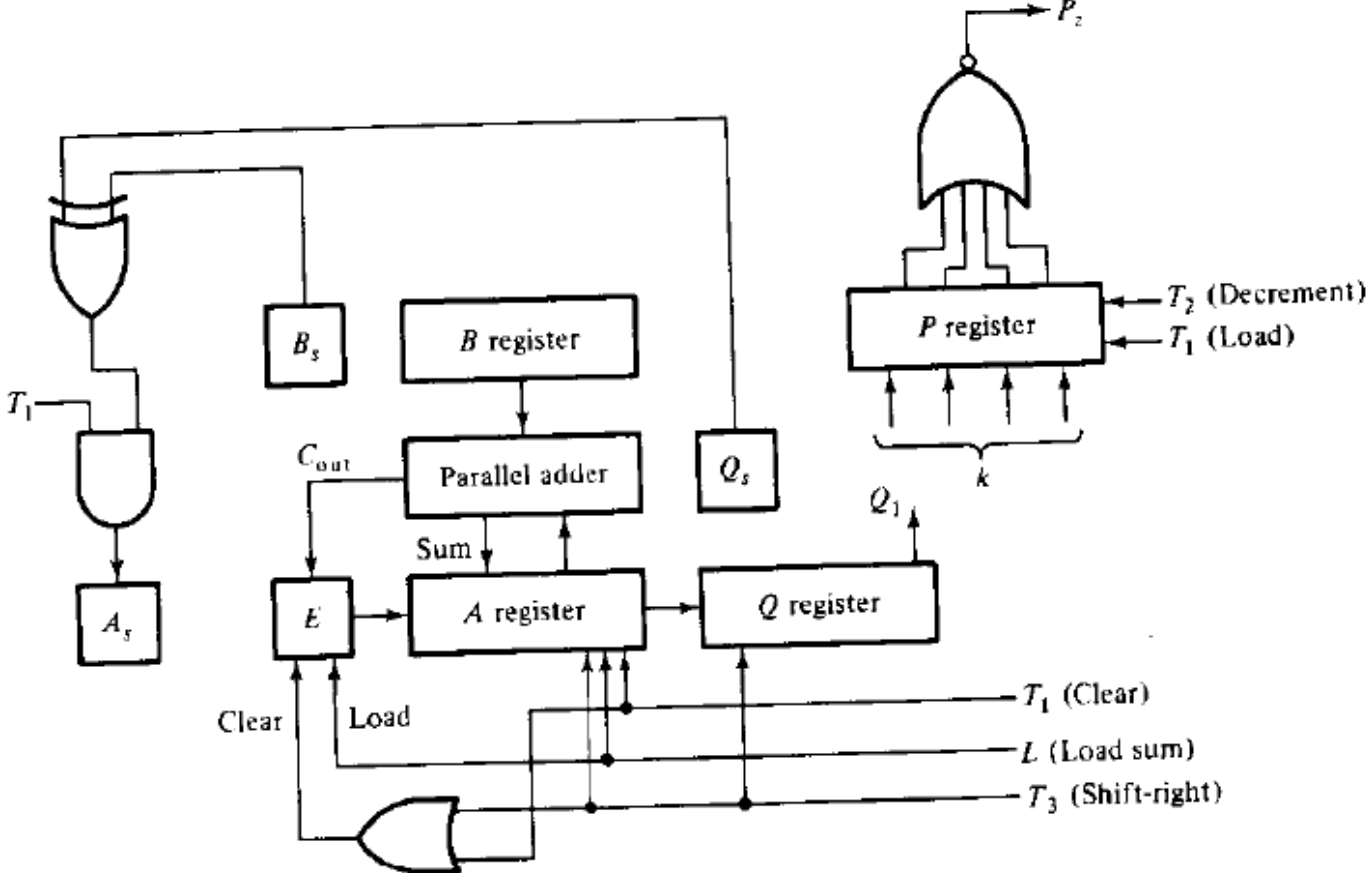
(a) State diagram

T_0 : Initial state
 T_1 : $A_s \leftarrow B_s \oplus Q_s, A \leftarrow 0, E \leftarrow 0, P \leftarrow k$
 $Q_1 T_2$: $A \leftarrow A + B, E \leftarrow C_{out}$
 T_2 : $P \leftarrow P - 1$
 T_3 : $AQ \leftarrow shr EAQ, E \leftarrow 0$




• Output from control logic:

 - **T0**-indicates that system in initial state
- **T1**-loads sign to A_s and k into P
- **T2**-decrements P ,
 - If $Q=1$, L generated- loads A (sum) and E
- **T3**-Shifts A, Q , clears E



 
- Design of hard wired control
 - 2 JK flipflops and 1 2x4 decoder can be used as there are 4 states



	Present State		Inputs		Next state		Flip-flop inputs			
	G_2	G_1	q_m	P_z	G_2	G_1	JG_2	KG_2	JG_1	KG_1
T_0	0	0	0	X	0	0	0	X	0	X
T_0	0	0	1	X	0	1	0	X	1	X
T_1	0	1	X	X	1	0	1	X	X	1
T_2	1	0	X	X	1	1	X	0	1	X
T_3	1	1	X	0	1	0	X	0	X	1
T_3	1	1	X	1	0	0	X	1	X	1

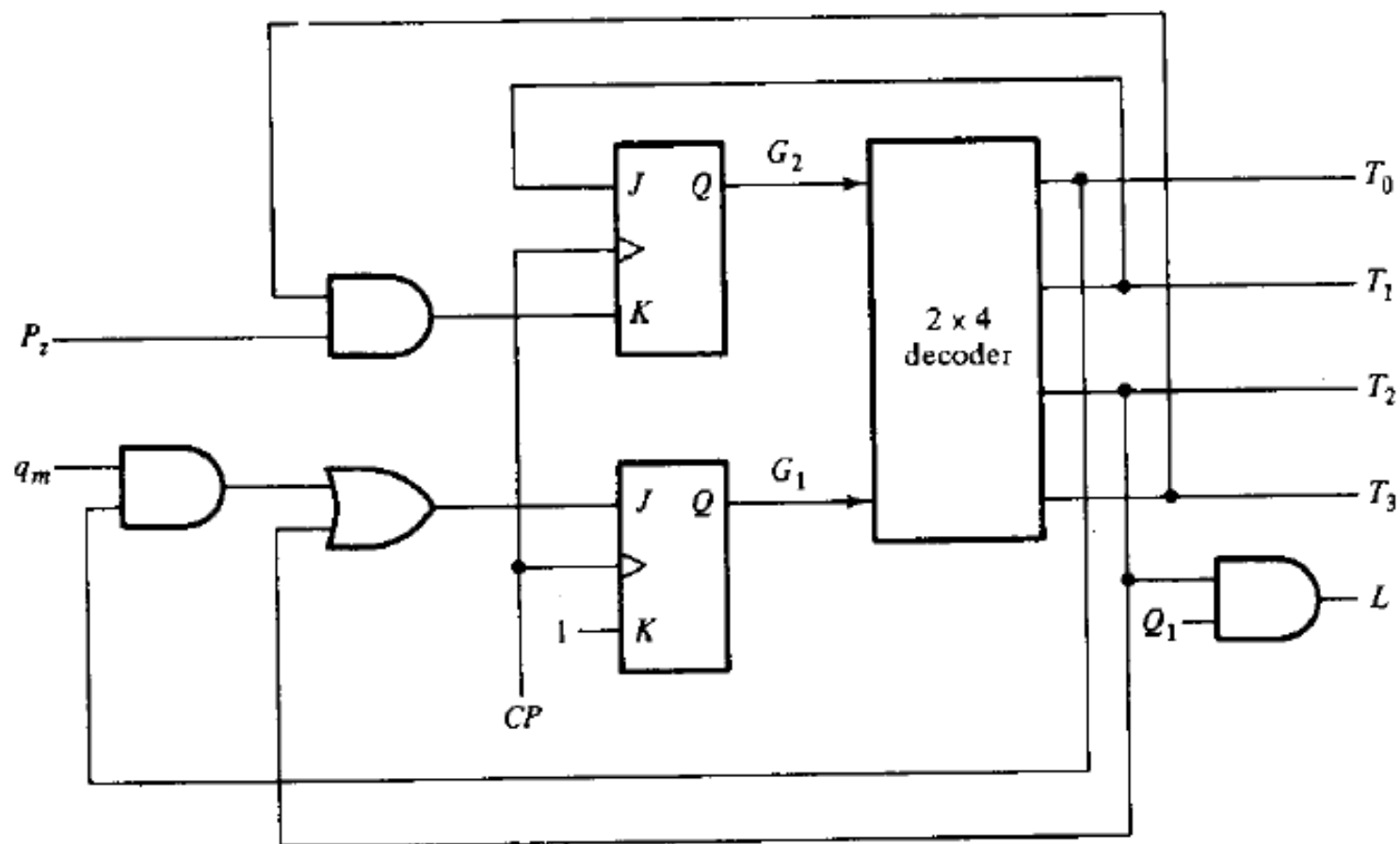(a) Excitation table

$$\begin{aligned}
 JG_2 &= T_1 & KG_2 &= T_3 P_z \\
 JG_1 &= T_0 q_m + T_2 & KG_1 &= 1
 \end{aligned}$$



3. Programmable Logic Array

- PLA replaces decoder and decision logic circuits
- Internal paths inside PLA are programmed according to program table
- Similar to sequence register and decoder method, except that all combinational circuits are implemented with PLA



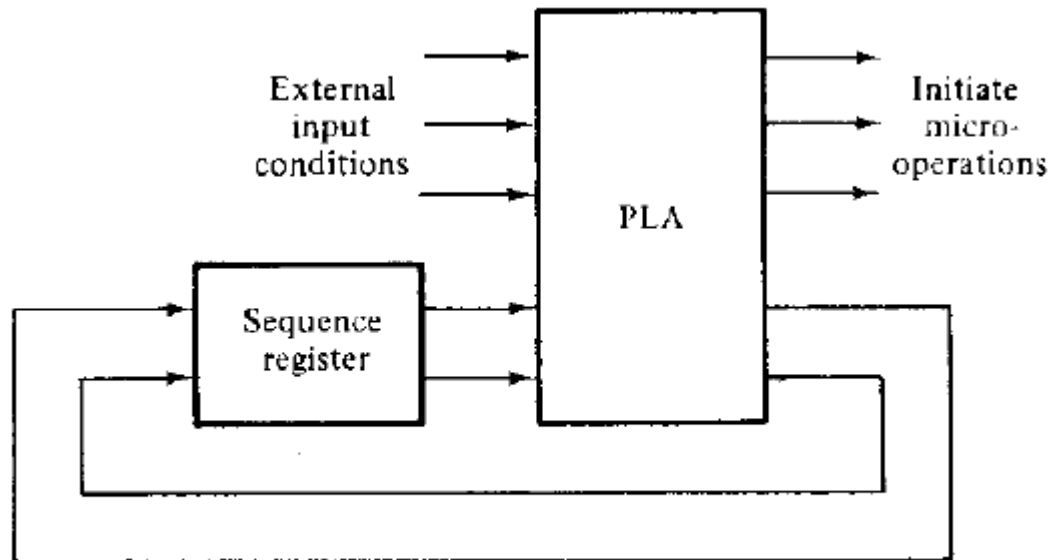


Figure 10-4 PLA control logic

PLA basics

 

 
- The AND and OR gates inside the PLA are initially fabricated with the links (fuses) among them
- The specific Boolean functions are implemented in sum of products form by opening appropriate links and leaving the desired connections.



 
Example(section 10.7)

- Design steps:
 1. Obtain state table for controller
(No of states determine the number of flipflops for sequence reg)
 2. Connect PLA to sequence register and to input and output variables
PLA program table obtained from state table

- Consider the example of binary multiplier





Present state		Inputs			Next state		Outputs				
G_2	G_1	q_m	P_2	Q_1	G_2	G_1	T_0	T_1	T_2	L	T_3
0	0	0	X	X	0	0	1	0	0	0	0
0	0	1	X	X	0	1	1	0	0	0	0
0	1	X	X	X	1	0	0	1	0	0	0
1	0	X	X	0	1	1	0	0	1	0	0
1	0	X	X	1	1	1	0	0	1	1	0
1	1	X	0	X	1	0	0	0	0	0	1
1	1	X	1	X	0	0	0	0	0	0	1

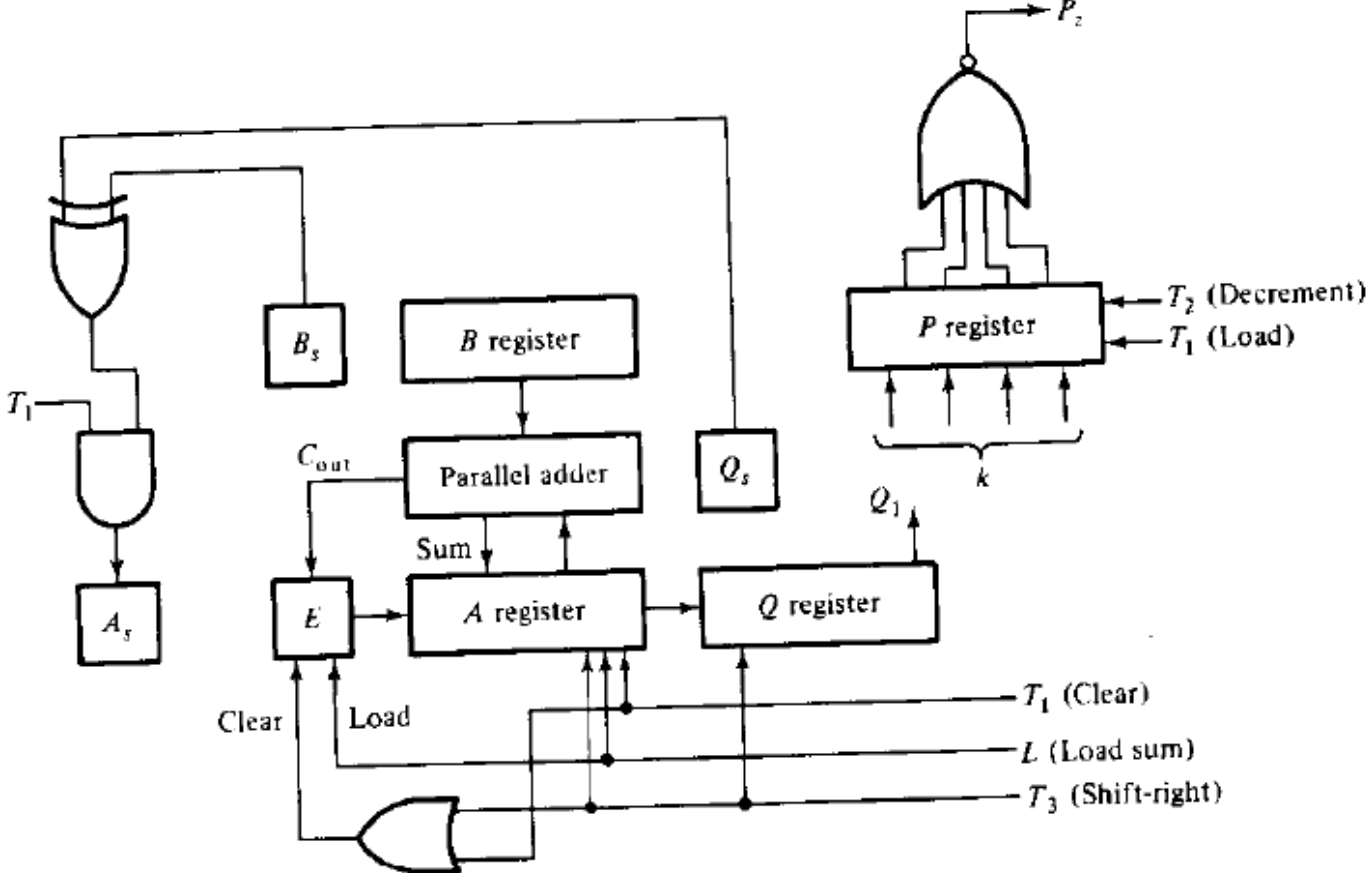

- Output from control logic:

 - **T0**-indicates that system in initial state
- **T1**-loads sign to A_s and k into P
- **T2**-decrements P ,
 - If $Q_1=1$, L generated- loads A (sum) and E
- **T3**-Shifts A, Q , clears E



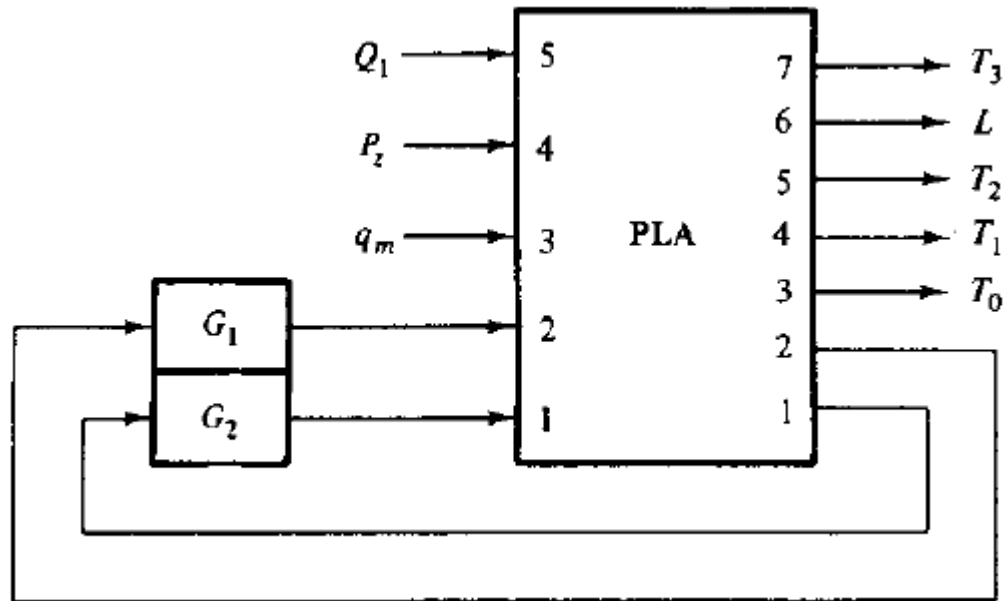

- **G1 and G2** –flipflops(sequence reg)
- **Input to PLA-** value of present state and 3 ext input

Product term	Inputs					Outputs							Comments
	1	2	3	4	5	1	2	3	4	5	6	7	
1	0	0	0	-	-	-	-	1	-	-	-	-	$T_0 = 1, q_m = 0$
2	0	0	1	-	-	-	1	1	-	-	-	-	$T_0 = 1, q_m = 1$
3	0	1	-	-	-	1	-	-	1	-	-	-	$T_1 = 1$
4	1	0	-	-	0	1	1	-	-	1	-	-	$T_2 = 1, Q_1 = 0$
5	1	0	-	-	1	1	1	-	-	1	1	-	$T_2 = 1, L = 1, Q_1 = 1$
6	1	1	-	0	-	1	-	-	-	-	-	1	$T_3 = 1, P_z = 0$
7	1	1	-	1	-	-	-	-	-	-	-	1	$T_3 = 1, P_z = 1$

Microprogrammed Control

- Control unit initiate a series of sequential steps of microoperations
- At any time certain operations are to be initiated and others idle
- So represented as series of 1's and 0's ->control word
- Microprogrammed-> CU whose control variables are stored in memory
- **Microinstruction**
- **Microprogram**
- **Control memory**


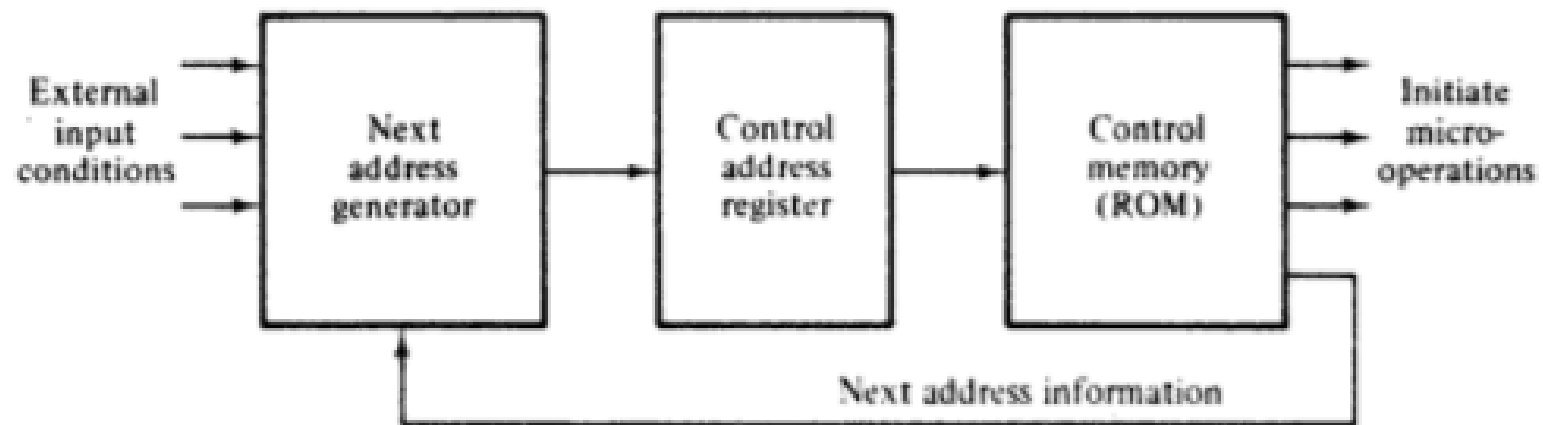


Figure 10-5 Microprogram control logic

Example(section 10.4)

- Problem statement: To design control logic for sign magnitude adder subtractor using microprogram control
- State in control memory- address of microinstruction

- Control state diagram

 

(a) State diagram

	Control outputs								
	x	s_2	s_1	s_0	C_{in}	L	y	z	w
T_0 : Initial state $x = 1$	1	0	0	0	0	0	0	0	0
T_1 : $B_s \leftarrow \bar{B}_s$	0	0	0	0	0	0	1	0	0
T_2 : nothing	0	0	0	0	0	0	0	0	0
T_3 : $A \leftarrow A + B$, $E \leftarrow C_{out}$	0	0	0	1	0	1	0	0	0
T_4 : $A \leftarrow A + \bar{B} + 1$, $E \leftarrow C_{out}$	0	0	1	0	1	1	0	0	0
T_5 : $E \leftarrow 0$	0	0	0	0	0	0	0	0	1
T_6 : $A \leftarrow \bar{A}$	0	1	1	1	0	1	0	0	0
T_7 : $A \leftarrow A + 1$, $A_s \leftarrow \bar{A}_s$	0	0	0	0	1	1	0	1	0

(b) Sequence of register transfers

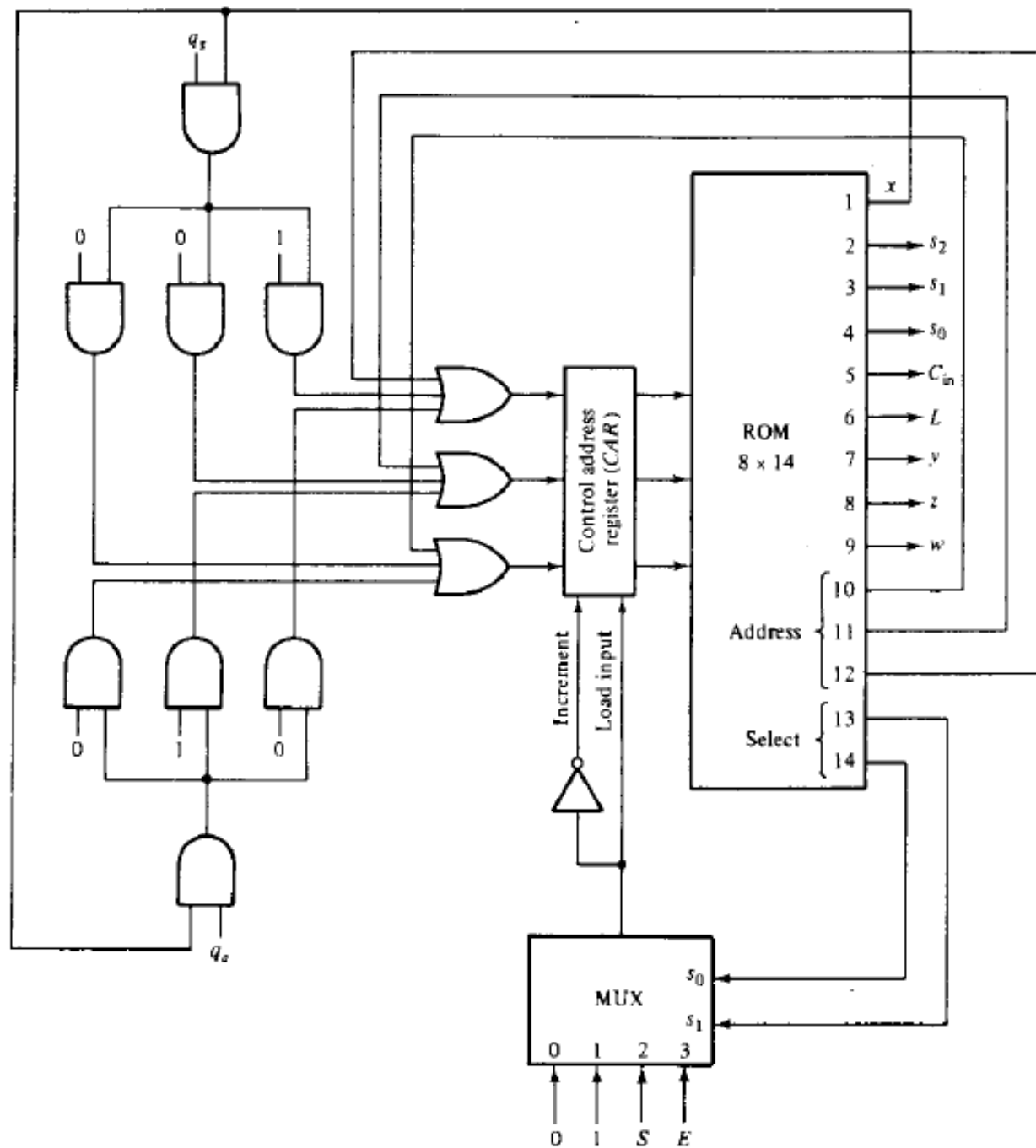



TABLE 10-2 Symbolic microprogram for control memory

ROM address	Microinstruction	Comments
0	$x = 1$, if ($q_s = 1$) then (go to 1), if ($q_a = 1$) then (go to 2), if ($q_s \wedge q_a = 0$) then (go to 0)	Load 0 or external address
1	$B_s \leftarrow \bar{B}_s$	$q_s = 1$, start subtraction
2	If ($S = 1$) then (go to 4)	$q_a = 1$, start addition
3	$A \leftarrow A + B$, $E \leftarrow C_{out}$, go to 0	Add magnitudes and return
4	$A \leftarrow A + \bar{B} + 1$, $E \leftarrow C_{out}$	Subtract magnitudes
5	If ($E = 1$) then (go to 0), $E \leftarrow 0$	Operation terminated if $E = 1$
6	$A \leftarrow \bar{A}$	$E = 0$, complement A
7	$A \leftarrow A + 1$, $A_s \leftarrow \bar{A}_s$, go to 0	Done, return to address 0

TABLE 10-3 Binary microprogram for control memory

ROM address	ROM outputs													
	x	s_2	s_1	s_0	C_{in}	L	y	z	w	<u>Address</u>			<u>Select</u>	
	1	2	3	4	5	6	7	8	9	10	11	12	13	14
0 0 0	1	0	0	0	0	0	0	0	0	0	0	0	0	1
0 0 1	0	0	0	0	0	0	1	0	0	0	1	0	0	1
0 1 0	0	0	0	0	0	0	0	0	0	1	0	0	1	0
0 1 1	0	0	0	1	0	1	0	0	0	0	0	0	0	1
1 0 0	0	0	1	0	1	1	0	0	0	1	0	1	0	1
1 0 1	0	0	0	0	0	0	0	0	1	0	0	0	1	1
1 1 0	0	1	1	1	0	1	0	0	0	1	1	1	0	1
1 1 1	0	0	0	0	1	1	0	1	0	0	0	0	0	1

Control of processor unit

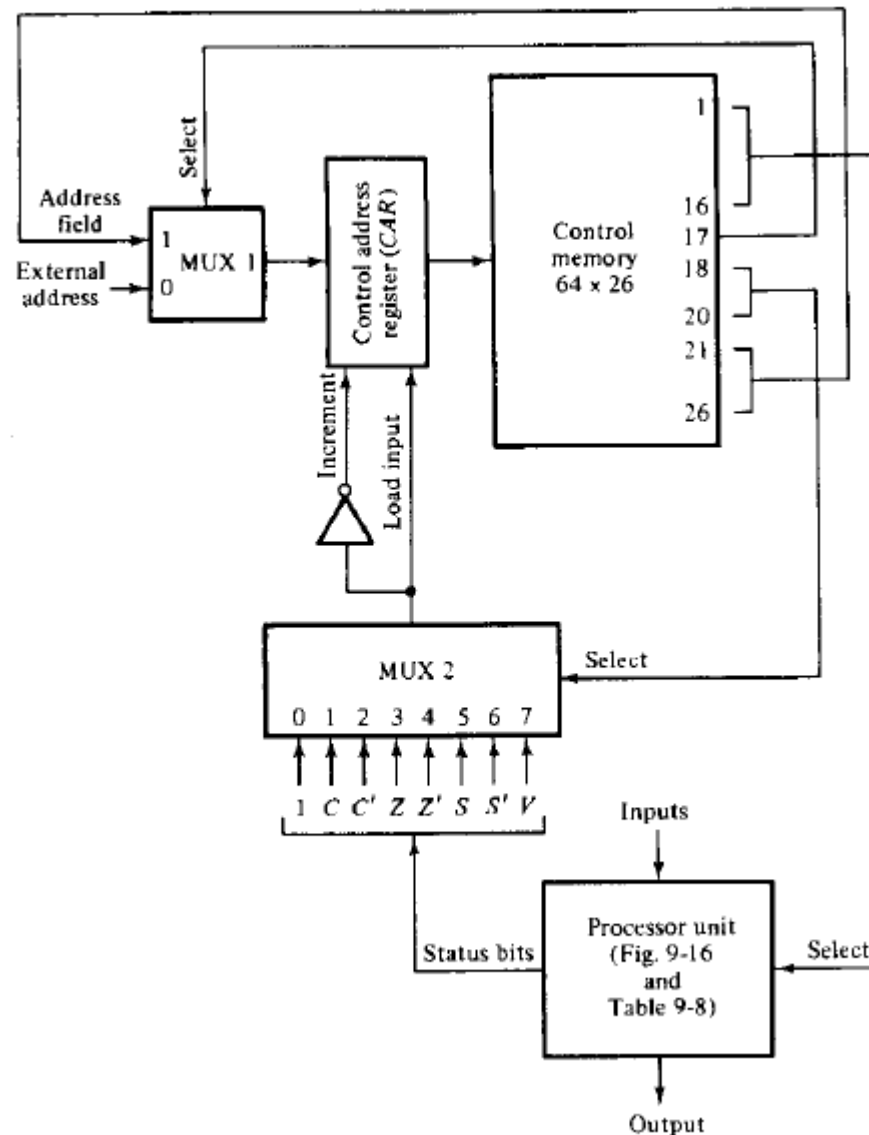

Example2

- Problem: counting no of 1's in register R1
- Algorithm:

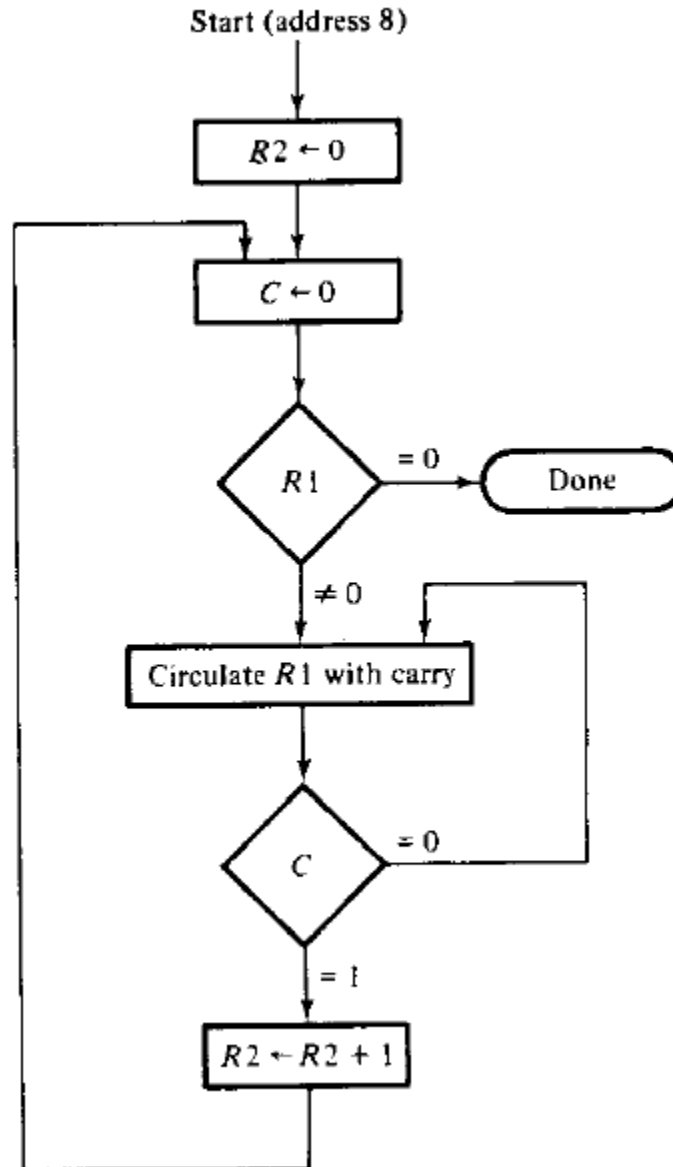



TABLE 10-4 Symbolic microprogram to count the number of 1's in $R1$


ROM address	Microinstruction	Comments
8	$R2 \leftarrow 0$	Clear $R2$ counter
9	$R1 \leftarrow R1, C \leftarrow 0$	Clear C , set status bits
10	If ($Z = 1$) then (go to external address)	Done if $R1 = 0$
11	$R1 \leftarrow \text{crc } R1$	Circulate $R1$ right with carry
12	If ($C = 0$) then (go to 11)	Circulate again if $C = 0$
13	$R2 \leftarrow R2 + 1$, go to 9	Carry = 1, increment $R2$

TABLE 10-5 Binary microprogram to count the number of 1's in $R1$

ROM address	ROM content														
	Microoperation select					MUX select				Address field					
	A	B	D	F	H										
	1				16	17		20		21				26	
001000	000	000	010	0000	011	1	0	0	0	0	0	1	0	0	1
001001	001	000	001	0000	000	1	0	0	0	0	0	1	0	1	0
001010	001	001	000	1000	000	0	0	1	1	0	0	0	0	0	0
001011	001	001	001	1000	101	1	0	0	0	0	0	1	1	0	0
001100	001	001	000	1000	000	1	0	1	0	0	0	1	0	1	1
001101	010	000	010	0001	000	1	0	0	0	0	0	1	0	0	1


Microprogram sequencer

- Microprogram CU  control memory
Next address generator
- Address generation part- sequencer
- Sequencer provide the following capabilities
 1. Increments the present address
 2. Branches to address specified in address field of microinstruction
 3. Branches to address if specified status bit is 1
 4. Transfers to new address specified by external source
 5. Has facility for subroutine calls and return

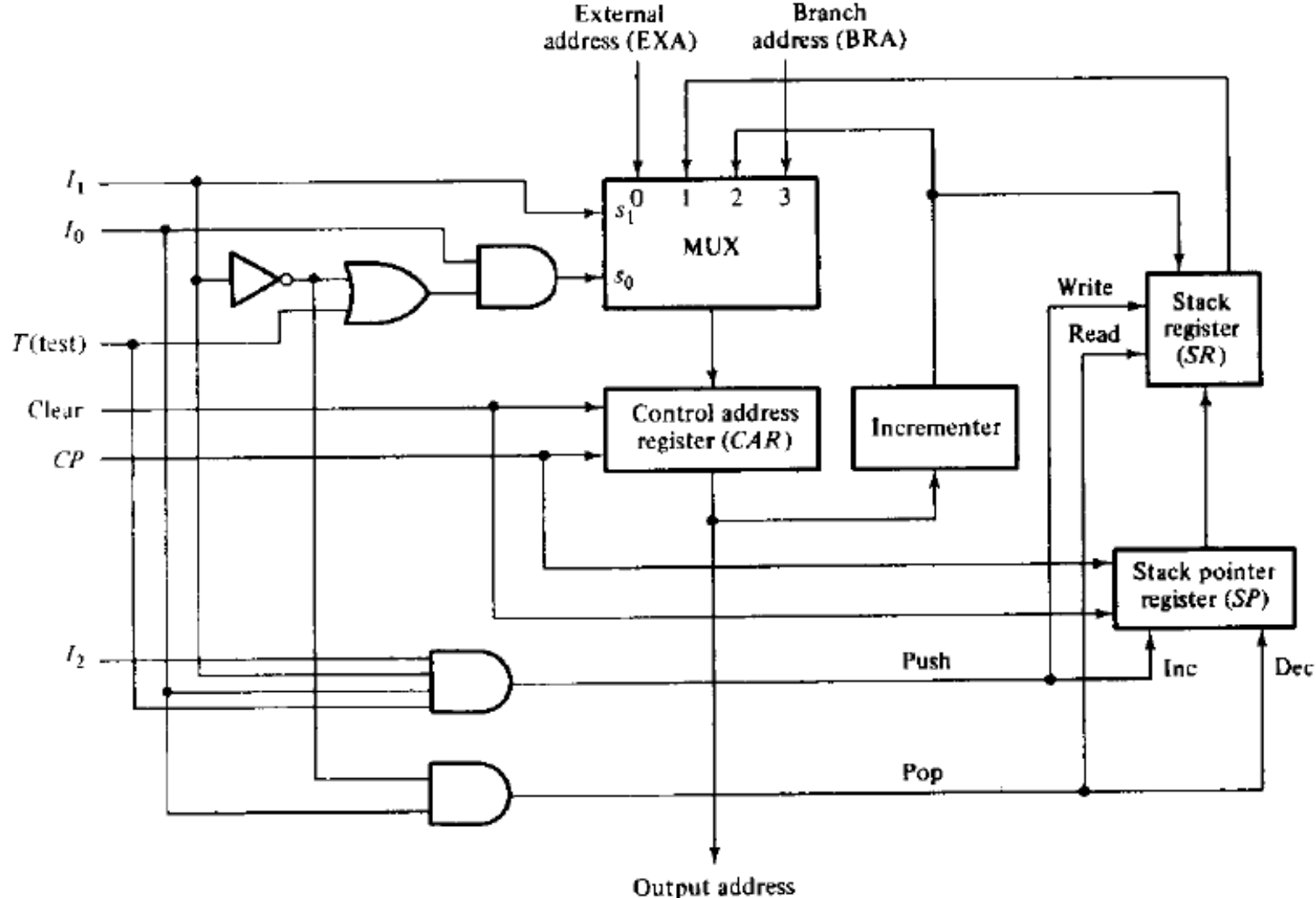


I_2	I_1	I_0	T	s_1	s_0	Operation	Comments
X	0	0	X	0	0	$CAR \leftarrow EXA$	Transfer external address
X	0	1	X	0	1	$CAR \leftarrow SR$	Transfer from register stack
X	1	0	X	1	0	$CAR \leftarrow CAR + 1$	Increment address
0	1	1	0	1	0	$CAR \leftarrow CAR + 1$	Increment address
0	1	1	1	1	1	$CAR \leftarrow BRA$	Transfer branch address
1	1	1	0	1	0	$CAR \leftarrow CAR + 1$	Increment address
1	1	1	1	1	1	$CAR \leftarrow BRA, SR \leftarrow CAR + 1$	Branch to subroutine

- Output from CAR- address of control memory
- I_2, T have no effect when $I_1 I_0 = 00, 01, 10$
- Conditional branch operation:
- When $I_1 I_0 = 11, I_2 = 0$
 - If $T=1$, sequencer branches to BRA(branch address from microinstruction)
 - If $T=0$, increments CAR
- Conditional subroutine call:
- When $I_2 I_1 I_0 = 111$
 - If $T=1$, CAR+1 pushed to stack, sequencer branches to BRA
 - If $T=0$, increments CAR
- Return from subroutine:
- When $I_1 I_0 = 01$
 - Pop stack – branch to address on top of stack

 

 (a) Call subroutine (push stack) $I_2 I_1 I_0 T = 1111$



(b) Return from subroutine (pop stack) $I_1 I_0 = 01$

Figure 10-20 Stack operations in microprogram sequencer

Microprogrammed CPU organization

- I - Sequence selector
- SL - MUX selector
- BRA - Branch address
- MC - Memory control
- PS - Processor selector
- DF - Data field

